

Current Copier based Mixed-Signal Multiplier for Machine Learning Applications

Guide: Prof. Rajesh Zele

Mihir Kavishwar (17D070004)

Advanced Integrated Circuits and Systems Lab
Electrical Engineering, IIT Bombay

Outline

- 1 Introduction
- 2 System Architecture
- 3 Current Copier Principle
- 4 Current Copier Based Multiplier
- 5 Sources of Error
- 6 Schematics and Simulation Results
- 7 Conclusion
- 8 References

Introduction

- Most Machine Learning algorithms can be characterized as a sequence of Matrix Vector Multiplications (MVMs) interposed with non-linear transforms

Introduction

- Most Machine Learning algorithms can be characterized as a sequence of Matrix Vector Multiplications (MVMs) interposed with non-linear transforms
- **Multiply and Accumulate** (MAC) is the fundamental operation which gets repeated in MVMs: $y_i = \sum_{j=1}^N w_{ij} \cdot x_j$

Introduction

- Most Machine Learning algorithms can be characterized as a sequence of Matrix Vector Multiplications (MVMs) interposed with non-linear transforms
- **Multiply and Accumulate** (MAC) is the fundamental operation which gets repeated in MVMs: $y_i = \sum_{j=1}^N w_{ij} \cdot x_j$
- For **Edge Device** applications where we need to operate at very **low power** but still get **high performance**, Analog/Mixed-Signal implementations of MAC are proving to be much better alternative to the Digital counterpart

Introduction

- Most Machine Learning algorithms can be characterized as a sequence of Matrix Vector Multiplications (MVMs) interposed with non-linear transforms
- **Multiply and Accumulate** (MAC) is the fundamental operation which gets repeated in MVMs: $y_i = \sum_{j=1}^N w_{ij} \cdot x_j$
- For **Edge Device** applications where we need to operate at very **low power** but still get **high performance**, Analog/Mixed-Signal implementations of MAC are proving to be much better alternative to the Digital counterpart
- In this work, I have explored a **Current-Copier based Mixed-Signal Multiplier** circuit in an attempt to come up with a novel implementation of MAC

System Architecture


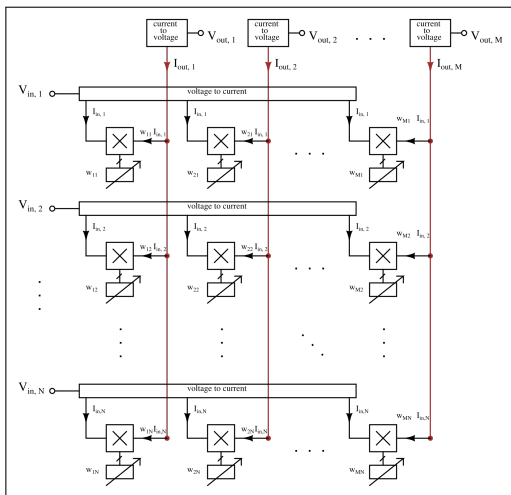


Figure: Mixed-Signal Matrix Vector Multiplier

$$\begin{bmatrix} I_{out,1} \\ I_{out,2} \\ \vdots \\ I_{out,M} \end{bmatrix} = \begin{bmatrix} w_{11} & w_{12} & \dots & w_{1N} \\ w_{21} & w_{22} & \dots & w_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ w_{M1} & w_{M2} & \dots & w_{MN} \end{bmatrix} \begin{bmatrix} I_{in,1} \\ I_{in,2} \\ \vdots \\ I_{in,N} \end{bmatrix}$$

- Weights are stored digitally in local registers while the input and output currents are Analog
- Same multiplier cell is replicated several times
- Connecting multiplier output currents in parallel gives us the addition operation

Current Copier Principle

 

Phase ϕ_1

- M acts as an **input** device with its gate and drain connected to input current source
- I_{in} charges C until V_{gs} reaches a value which corresponds to $I_{in} = I_{ds}$

Figure: Basic Current Copier Cell

Current Copier Principle

 


Figure: Basic Current Copier Cell

Phase ϕ_1

- M acts as an **input** device with its gate and drain connected to input current source
- I_{in} charges C until V_{gs} reaches a value which corresponds to $I_{in} = I_{ds}$

Phase ϕ_2

- M acts as an **output** device with its drain disconnected from gate and connected to output node
- M sinks I_{out} which is controlled by same V_{gs} and thus equal to I_{in}

Current Copier Based Multiplier

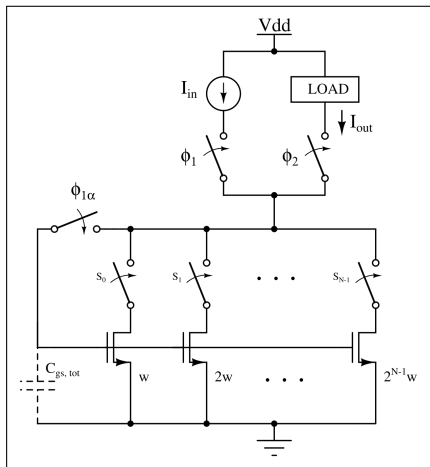


Figure: Multiplier Cell

Assuming V_{gs} remains constant across the 2 phases,

$$I_{out, \phi_2} = w \times I_{in, \phi_1}$$

where,

$$w := \frac{2^0 \cdot S_{0, \phi_2} + 2^1 \cdot S_{1, \phi_2} + \dots + 2^{N-1} \cdot S_{N-1, \phi_2}}{2^0 \cdot S_{0, \phi_1} + 2^1 \cdot S_{1, \phi_1} + \dots + 2^{N-1} \cdot S_{N-1, \phi_1}}$$

 


Figure: Possible values of w for $N = 3$

Current Copier Based Multiplier - Alternate Architecture


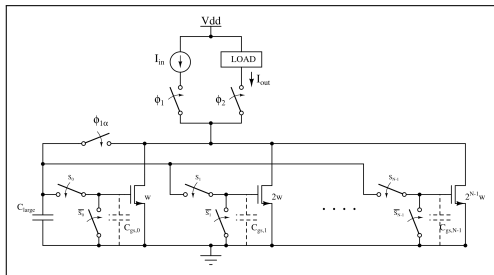


Figure: Alternate architecture of Multiplier Cell

- While avoiding switches in current path, this architecture brings other problems
- The net value of gate capacitor depends heavily on the configuration of switches
- A large external capacitor needs to be connected at the gate which results in more charging time and hence lesser speed


Sources of Error

- Gate Switch Charge Injection

 


Sources of Error

 - Gate Switch Charge Injection
 - Dummy switch compensation




Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough




Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches




Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation




Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation
 - ▶ Cascode configuration and larger channel length



Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation
 - ▶ Cascode configuration and larger channel length
- Incomplete settling of Gate Voltage




Sources of Error

- Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation
 - ▶ Cascode configuration and larger channel length
- Incomplete settling of Gate Voltage
 - ▶ Either increase input current range or decrease operating frequency

Sources of Error

 - Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation
 - ▶ Cascode configuration and larger channel length
- Incomplete settling of Gate Voltage
 - ▶ Either increase input current range or decrease operating frequency
- Junction Leakage



Sources of Error

- Gate Switch Charge Injection
 - ▶ Dummy switch compensation
- Drain Switch Charge Feedthrough
 - ▶ Complementary switches
- Channel Length Modulation
 - ▶ Cascode configuration and larger channel length
- Incomplete settling of Gate Voltage
 - ▶ Either increase input current range or decrease operating frequency
- Junction Leakage
 - ▶ Don't leaving gate capacitor floating for a long time

Schematics

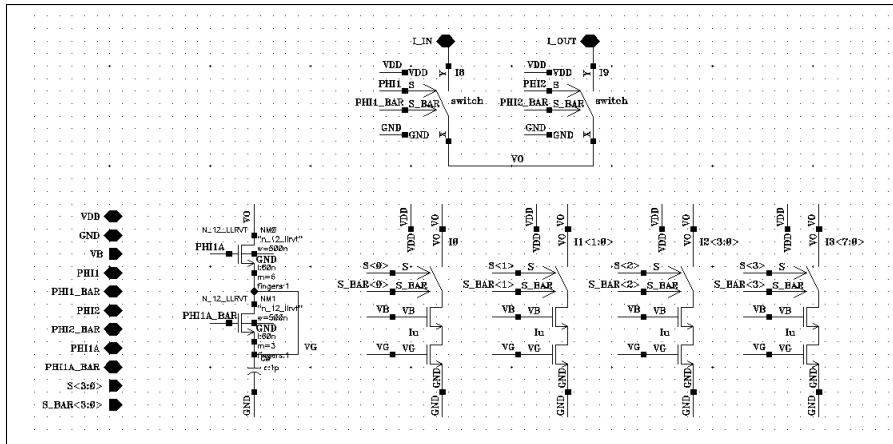


Figure: Final schematic of 4-bit Current Copier Multiplier

Schematics

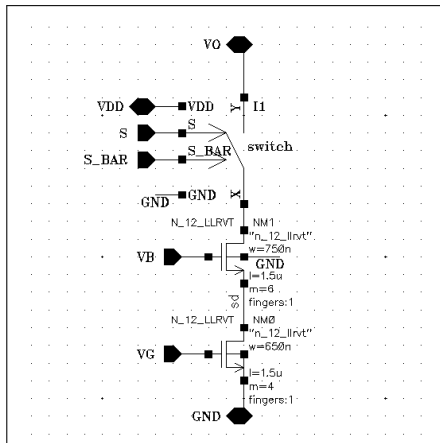


Figure: Unit Cell

 


Figure: Complementary Switch

Testbench

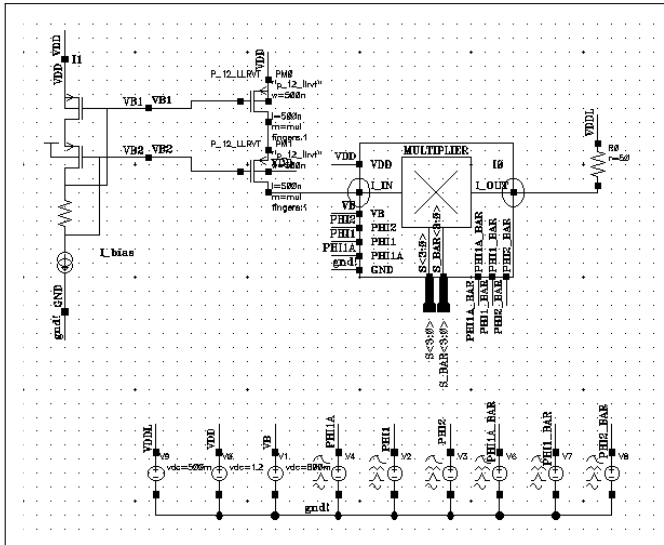


Figure: 4-bit Multiplier Testbench

Simulation Results

 


Figure: Transient Analysis with w varying from 1 to 15

Simulation Results

 


Figure: I_{out} value in phase ϕ_2 with w varying from 1 to 15 for different I_{in}

Simulation Results

 


Figure: Error Analysis

Simulation Results

 


Figure: Average Power vs Input Current

For input current range of 500nA to 5 μ A, average power consumed by multiplier plus biasing circuit is **2.5 μ W** to **13 μ W**

Simulation Results

 


Figure: Transient Analysis with fractional w

Weight	$I_{out,actual} (\mu A)$	$I_{out,ideal} (\mu A)$	% Error
$2/2 = 1$	4.994	5	0.12
$1/2 = 0.5$	2.484	2.5	0.64
$1/3 = 0.333$	1.648	1.667	1.14
$2/3 = 0.667$	3.314	3.333	0.58
$1/4 = 0.25$	1.231	1.25	1.52
$3/4 = 0.75$	3.731	3.75	0.51
$7/2 = 3.5$	17.978	17.5	2.73

Table: Error Analysis with fractional w for $I_{in} = 5 \mu A$

MAC Testbench

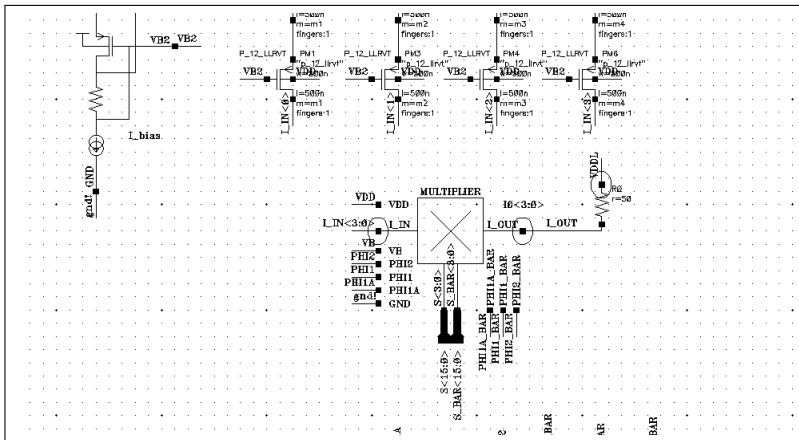


Figure: 4 Multipliers connected in parallel for testing MAC operation

Simulation Results

 


Figure: MAC Transient Simulation




w_1	$I_{in,1}$ (μA)	w_2	$I_{in,2}$ (μA)	w_3	$I_{in,3}$ (μA)	w_4	$I_{in,4}$ (μA)	$I_{out,actual}$ (μA)	$I_{out,ideal}$ (μA)	% Error
8	3	2	1.5	11	4	4	1	78.506	75	4.675
4.667	3	10	1.5	6	4	1.5	1	56.621	54.5	3.892

Table: MAC Error Analysis

Conclusion

- A new architecture of Mixed-Signal Multiplier based on Current-Copier principle was explored
- The 4-bit Multiplier operating at 1 MHz consumes $< 13 \mu\text{W}$ power and has $< 7\%$ output error for input current range of 500 nA - 5 μA
- Achieving high resolution is difficult with this architecture due to input dependent charge feedthrough from drain switches
- Future work includes:
 - ▶ Exploring ways to increase multiplier speed, resolution of weights and support for negative weights
 - ▶ Incorporating transistor level design in place of behavioural models in the image classifier system
 - ▶ Designing storage elements and circuits for non-linear transforms

References

-  S.J. Daubert, D. Vallancourt. and Y.P. Tsvividis, “**Current Copier Cells**”, Electronics Letters, vol. 24, no. 25, pp. 1560-1562, 8 Dec. 1988.
-  D. Vallancourt, Y. P. Tsvividis and S. J. Daubert, “**Sampled-current circuits**,” IEEE International Symposium on Circuits and Systems,, 1989, pp. 1592-1595 vol.3, doi: 10.1109/ISCAS.1989.100665.
-  W. Groeneveld, H. Schouwenaars and H. Termeer, “**A self calibration technique for monolithic high-resolution D/A converters**,” IEEE International Solid-State Circuits Conference, 1989 ISSCC. Digest of Technical Papers, 1989, pp. 22-23, doi: 10.1109/ISSCC.1989.48217.